

Total No. of Questions : 8]

SEAT No. :

P 3272

[Total No. of Pages : 4

[5353] - 145
TE (Electronics)
NETWORK SYNTHESIS
(2012 Pattern)

Time : 2:30 Hours]

[Max. Marks :70

Instructions to the candidates:

Answer Q1 or Q2, Q3 or Q4, Q5 or Q6, Q7 or Q8.

Q1) a) Synthesize function using Foster forms. **[6]**

$$Z(s) = \frac{s(s^2 + 4)}{2(s^2 + 1)(s^2 + 9)}$$

b) Realize network function, with 1Ω termination. **[6]**

$$Z(s) = \frac{1}{(s^3 + 3s^2 + 3s + 2)}$$

c) Prove that $\frac{V_2}{V_g} = \frac{1}{2} \frac{R - Z_a}{R + Z_a}$ of constant resistance lattice, whose source and load impedance are equal to R. **[8]**

OR

Q2) a) Explain elementary synthesis concepts **[6]**

- i) Removal of pole at infinity
- ii) Removal of pole at origin
- iii) Removal of conjugate imaginary poles

b) Determine range of K in P (s) so that given polynomials are hurwitz. **[6]**

- i) $P(s) = s^3 + 20s^2 + 5s + 10K$
- ii) $P(s) = s^4 + 25s^3 + 15s^2 + 20s + K$

P.T.O

c) Test whether following functions are positive real function or not. [8]

i)
$$F(s) = \frac{3s^2 + 5}{s^3 + s}$$

ii)
$$P(s) = \frac{2s^2 + 2s + 1}{s^3 + 2s^2 + s + 2}$$

Q3) a) Explain frequency and impedance scaling with suitable example. [6]

b) State properties of Butterworth approximation. [4]

c) Determine transfer function of Chebyshev low pass filter to meet the following specification. [6]

i) 1dB ripple in the pass band

ii) Cut off frequency $\omega_c = 10 \times 10^5 \text{ rad/sec}$

iii) The magnitude must be down to 25dB at $\omega = 3 \times 10^6 \text{ rad/sec}$


OR

Q4) a) Compare Butterworth and Chebyshev Approximation Techniques. [4]

b) Determine transfer function and realize low pass Butterworth approximation filter whose requirements are characterized by, [6]

$$A_{\max} = 1\text{dB}, A_{\min} = 30\text{dB}, \omega_s = 350\text{rad/sec}$$

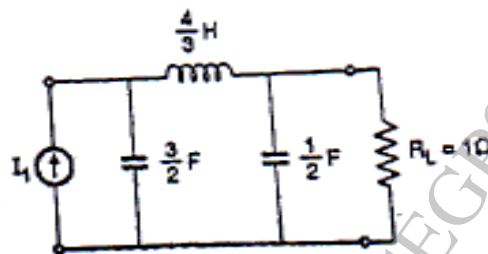c) Normalized third order low pass filter is shown below in figure [6]



Design c) $\omega_c = 10^6 \text{ rad/sec}$ and the impedance load of 500Ω

Q5) a) Design 2nd order Sallen and key high pass Butterworth filter having


cutoff frequency of $300H_z$ [4]

- b) Explain the different biquad feedback topologies used in active filter designing and list the important observations [6]
- c) Synthesize the following high pass filter function using RC-CR transformation. [6]

$$H(s) = \frac{Ks^3}{s^2 + s + 36}$$

OR

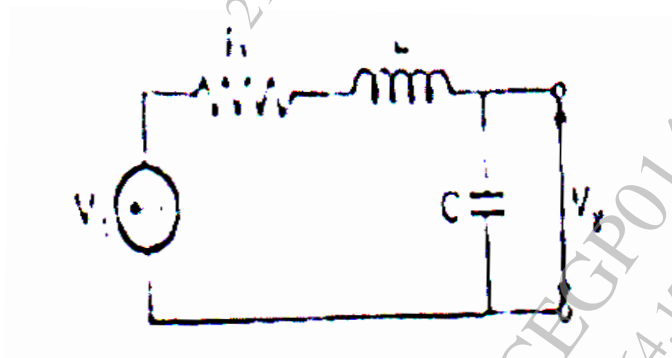- Q6)** a) Differentiate between passive and active filters. [4]
- b) Synthesize 2nd order active low pass Butterworth filter to have a cut off frequency of 159.15KHz then using RC-CR transformation, realize with same cut off frequency. [6]
- c) What are the advantages and disadvantages of Active filter? [6]
- Q7)** a) For the series RLC circuit shown in figure, Calculate the sensitivities of K, the resonant frequency ω_p , the quality factor Q_p with respect to R, L and C. Comment on the obtained result. [6]




b) Prove the following sensitivity relationships [6]

i) $S_x^{P^n} = nS_x^P$

ii) $S_{\sqrt{x}}^P = 2S_x^P$

iii) $S_x^{y+c} = \frac{y}{y+c} S_x^y$

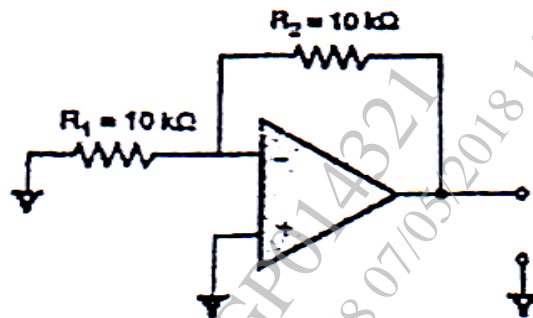c) The op-amp used in the inverting circuit in figure, has an input bias current of 600nA and an input offset current that can range between ± 100 nA. Find the resulting maximum output offset voltage. [6]



OR

Q8) a) Define sensitivity, Give some of its important properties. [4]

b) Explain the concept of gain sensitivity. also explain the various factors affecting the gain sensitivity. [6]

c) Explain effect of the following op-amp characteristics on the active filter. [8]

- i) Input offset voltage
- ii) Input bias current
- iii) Slew rate
- iv) CMRR

